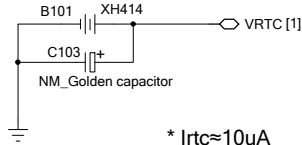


Moudle Design


Charge golden capacitor or battery when VBAT is applied.

If unused, keep VRTC open.




* As only powering the VRTC pin to keep the RTC will lead an error about 5 minutes a day, it is recommended to power VBAT and VRTC pin at the same time when RTC function is needed. For more details, please refer to M66 HD.

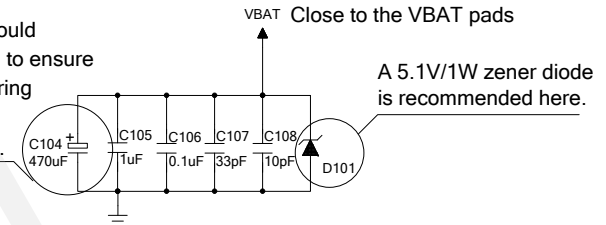Capacitance of C104 should be chosen by debugging to ensure the max voltage drop during the burst transmission does not exceed 400mV.




- VBAT ranges from 3.3V to 4.6V.
- Module drains the maximum current around 1.6A in burst time (577us).
- The width of VBAT trace is recommended to be more than 2mm.
- Capacitance is arranged in ascending order, the smallest one closes to the VBAT pad, and keep all capacitance as close to the VBAT pad as possible.

Reference circuit of ADC

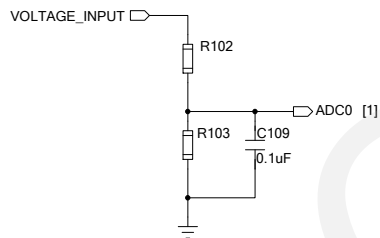

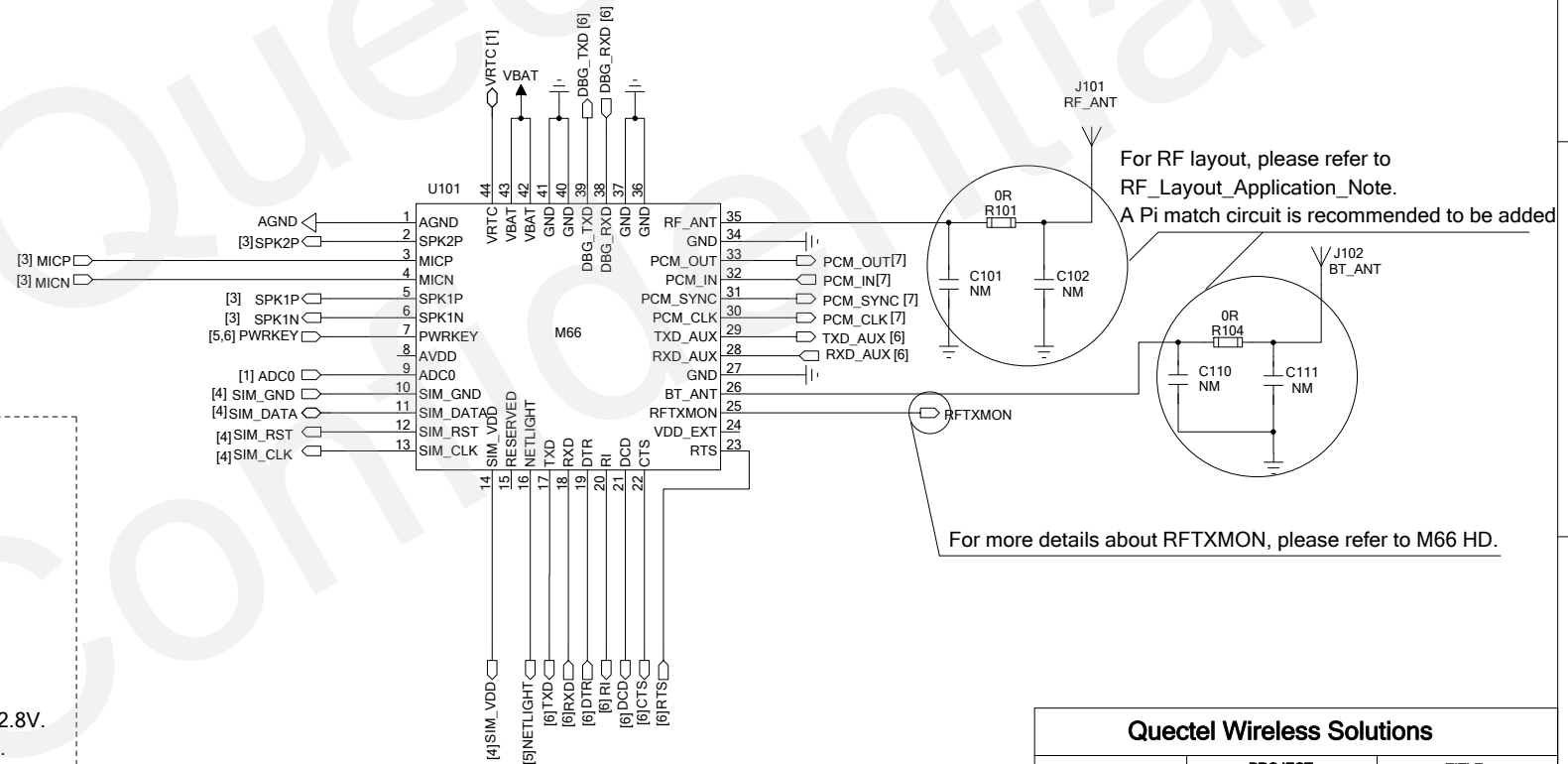- * The voltage range of ADC input channel is 0 to 2.8V.
- * Please select a high-precision divider resistance.



Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER V1.02
SHEET	1 OF 7	DATE 2014-12-5


Power Supply

NOTE

The voltage converter should provide current at least 2.0A.


LDO Application

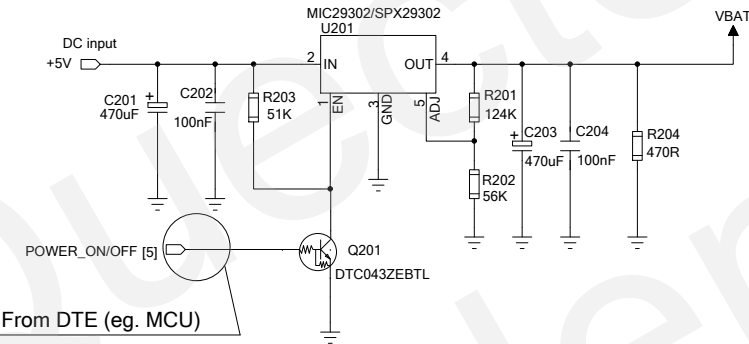It is used when the DC input voltage is below 7V.



DC-DC Application

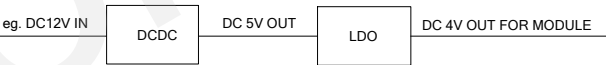1. It can be used when the input voltage is above 7V in vehicle application.
2. Use DCDC to convert high input voltage to 5V and LDO will generate 4V typical voltage for the module.



Quectel Wireless Solutions


DRAWN BY Felix YIN	PROJECT M66	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER V1.02
SHEET	2 OF 7	DATE 2014-12-5

Audio Design


NOTES

1. AGND is recommended to be routed separately.
2. 10pF & 33pF capacitors are used for filtering TDD noise.
3. AIN has bias voltage of microphone.
4. Both AOUT1 and AOUT2 are capable of driving 32ohm load.
5. These components are used to enhance the ESD performance of MIC lines, it is strongly recommended to reserve them.


Hands-free Application of AIN/AOUT2

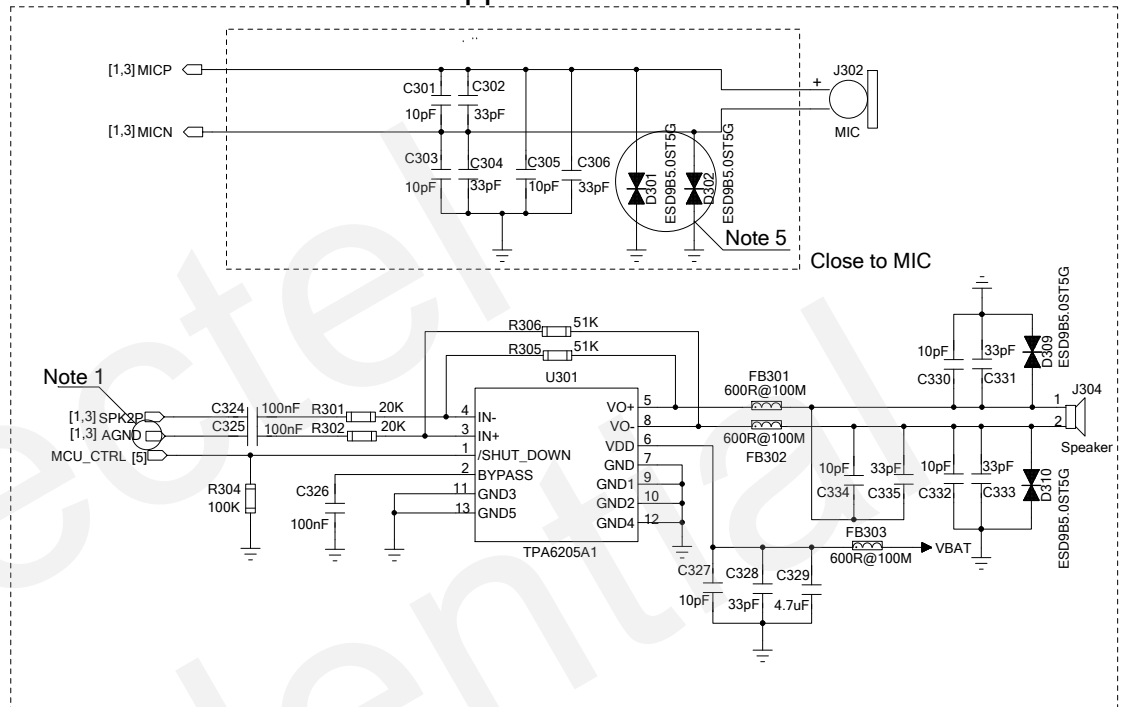

Handsets Application of AIN/AOUT1

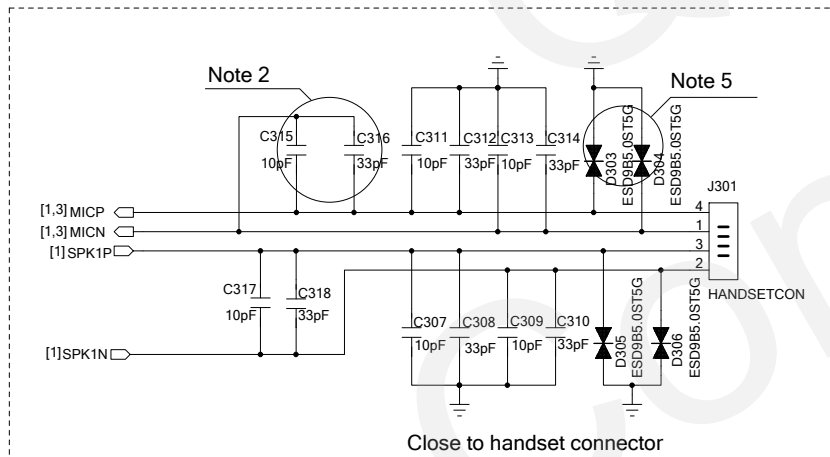

Earphone Application of AIN/AOUT2

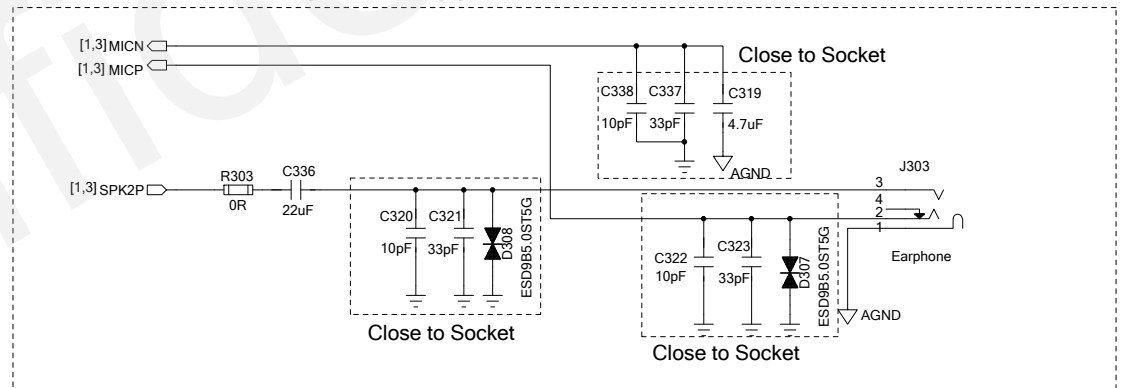


Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER V1.02
SHEET	3 OF 7	DATE 2014-12-5

SIM Card

SIM Card Interface

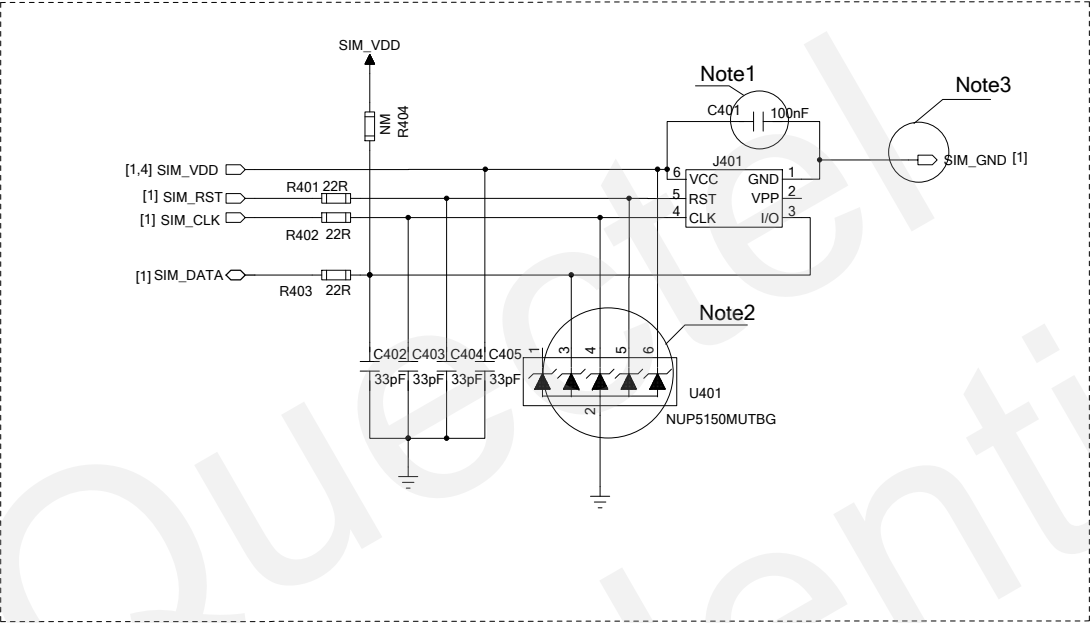


NOTES

- 1. The value of C401 should be less than 1uF.
- 2. U401 is used for protecting SIM card against ESD, and the junction capacitance should be less than 50pF. It should be placed nearby SIM card holder J401.
- 3. For M66 module, Ground of SIM card is recommended to be routed to the Pin 10 ("SIM_GND") of the module separately.

Quectel Wireless Solutions		
DRAWN BY Felix YIN	PROJECT M66	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER V1.02
SHEET	4 OF 7	DATE 2014-12-5

Drive


Turn On/Off

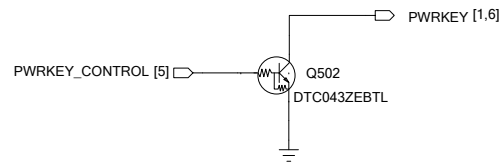

Recommended circuit for turning on/off the module.


LED Indication

Iout_max=4mA

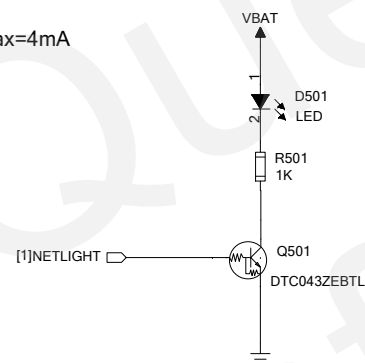

Pin "NETLIGHT" indicates the network status.

MCU GPIO

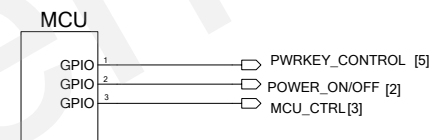

Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER V1.02
SHEET	5 OF 7	DATE 2014-12-5

Serial Interface

Electric characteristics of module's input and output port:

$VOH_{min}=0.85 \times VDD_EXT$

$VOL_{max}=0.15 \times VDD_EXT$


$VIL_{max}=0.25 \times VDD_EXT$

$VIH_{min}=0.75 \times VDD_EXT$

$VIH_{max}=VDD_EXT+0.2V$


$VDD_EXT=2.8V$ (typical value)

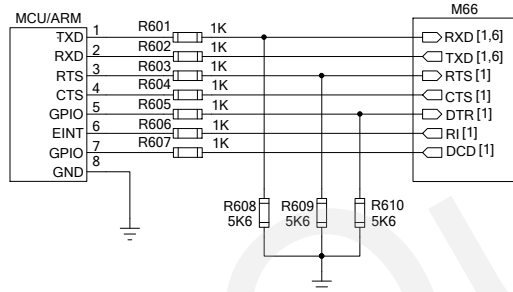Connection of All Functional UART Port for 3.3V System




NOTES

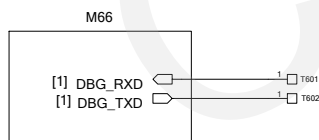1. CTS&RTS will be used for HW flow control when mass data has been sent.
2. When AT+QSCLK=1 is set on the module, customer's application can control the module to enter into or exit from the sleep mode through the pin DTR. When DTR is set to high level, and there is no on-air or hardware interrupt, such as GPIO interrupt or data on serial port, the module will enter into sleep mode automatically.
3. RI will output an indication signal when activity such as voice call or SMS is coming.
4. DCD is mainly applied in modem communication (PPP), the active status represents the communication link has been set up.
5. Please pay attention to the level match of UART in product application.




It is recommended to reserve the points for debug port.

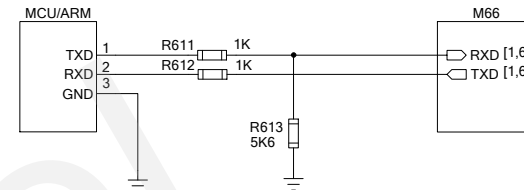Connection of Three-line UART Port for 3.3V System




* Please pay attention to the level match of UART in product application.

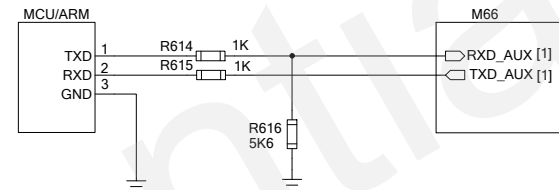Connection of Three-line AUX_UART Port for 3.3V System



* Please pay attention to the level match of UART in product application.

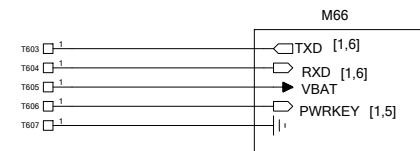It is recommended to reserve the points for upgrading the firmware.




* Please pay attention to the level match of UART in product application.

Quectel Wireless Solutions

DRAWN BY Felix YIN	PROJECT M66	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER V1.02
SHEET	6 OF 7	DATE 2014-12-5

PCM Design

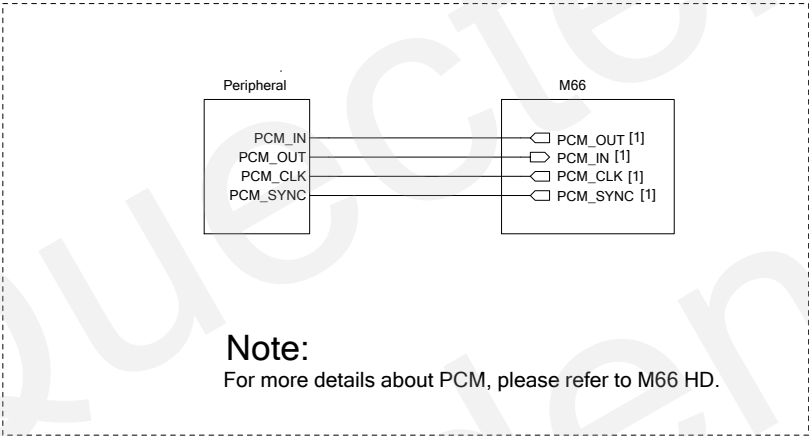

Note:

For more details about PCM, please refer to M66 HD.

Quectel Wireless Solutions		
DRAWN BY Felix YIN	PROJECT M66	TITLE Reference Design
CHECKED BY Tony GAO	SIZE A2	VER V1.02
	SHEET 7 OF 7	DATE 2014-12-5